



# Brookfield Primary School Knowledge Organiser



## Year 4: Electricity

Science is the study of the world around us through observation, description, investigation and experimentation.

### Key Facts

1. A series circuit contains a power source (cell or battery), wires and a component that requires electricity to work (bulb, bell or buzzer) in a single loop.
2. Electricity flows through the wires from the power source, around the circuit and back to the power source.
3. A switch can be added to the circuit to break or reconnect it.


### Conductors and Insulators

- Materials that allow electricity to pass through to create a complete circuit are called electrical conductors.
- Materials that do not allow electricity to pass through and do not complete a circuit are called electrical insulators.




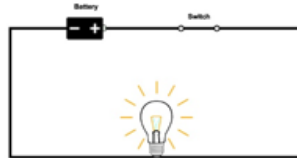
### Complete and Incomplete circuits

A complete circuit contains a power source, wires, and a component. They are connected in a loop with no breaks so that the electricity can flow from one end of the power source to the other.



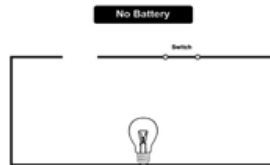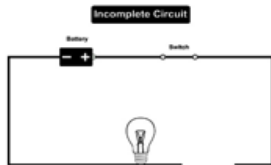The circuits below will not work. They are incomplete circuits.



### Electrical Components

-  cell/battery
-  wire
-  bulb/lamp
-  buzzer
-  switch

<b>battery</b>	A source of electrical energy made up of multiple cells.
<b>bulb</b>	Produces light in a circuit; can also be called a lamp.
<b>cell</b>	A single unit that is a source of electrical energy in a circuit.
<b>electricity</b>	Energy that powers electrical appliances and devices.
<b>electrical conductor</b>	A material which allows electricity to flow through it easily.
<b>electrical insulator</b>	A material that doesn't let electricity pass through it easily.
<b>series circuit</b>	A type of electrical circuit where the components are connected in a single loop.
<b>switch</b>	A component within a circuit which allows the flow of electricity to be turned on and off.

### General Scientific Words

Investigate, observe, explore, experiment, group, record, analyse.

Explore electrical appliances and electrical safety.

Learn about electrical components in a series circuit.

Investigate electrical circuits.

Explore conductors and insulators.

Learn about electrical switches.

Apply knowledge of conductors and insulators.

